We stern Electric Co., Incorporated, Engineering Dept., New York. (4 Pages) Page #1. Issue 1 - BT-438465. February 20, 1920.

voluce connected and at Parc

METHOD OF OPERATION TELEPHONE CIRCUIT

With Single Ended Cord - For Listening And Monitoring - With Repeating Coil Monitoring Feature - Arranged For Machine Ringing And - For Dialing Full Mechanical Office - Special Chief Operator's Desk.

THE SOUTHWESTERN TELEPHONE AND TELEGRAPH COMPANY
MAIN OFFICE. KANSAS CITY. MISSOURI.

proposed in the receiver when the elecate through the 375 and 354-0 regions

GENERAL DESCRIPTION

- 1. This circuit is used at a special chief operator's desk to provide the desk operator with a means of communicating with subscribers and other operators. It is arranged for repeating coil monitoring, listening, and dialing, and for cutting off ringing current automatically when machine ringing is used. It is equipped with a ringing key and with a flashing key. It is also provided with an operator's set and a desk stand so arranged that the operator's set may be used alone or the head receiver may be used with the desk stand transmitter.
- 2. When the plug of this circuit is inserted in a monitoring jack, the operator can monitor on the connection with all keys normal. If the trunk, talking or holding key is operated at this time, the telephone set is automatically disconnected from the monitoring circuit. To make a call over a ring down trunk, the plug of this circuit is inserted in the trunk jack and the ringing key operated. The telephone set is bridged across the trunk by the operation of the talking key. If the call is made over an automatic trunk, the talking key is operated and the desired number dialed. In the case of a ringdown tie trunk, the talking and ringing keys are both operated.

.100 pand empired and to said at atmember big days !-.

acted a read MD-05% is to see out its by no licencade at been ed

DETAILED DESCRIPTION

OPERATION

3. When a call over a key ended trunk is answered, the talking key associated with the lighted trunk lamp is operated bridging the B75 relay across the trunk in series with the winding of the #54-D retardation coil and shunted by the other winding, thereby tripoing machine ringing. The B75 relay operates, closing a circuit through the E249 relay and the special #178 relay per D-10866. At this time the E249 relay being the reverse of the special #178 relay in that it is quick to operate and slow to release, operates, disconnecting the winding of the E106 relay from its break contact. When the special #178-relay operates, the E249 relay releases and the circuit is closed to operate the E106 relay in series with the E179 relay. The E179 relay operated disconnects generator and ground from the leads of the ringing key associated with the cord, while the El06 relay operated disconnects the receiver from the #27 repeating coil and connects it to the #24 induction coil. The circuit is arranged in this way so that the interval between the operation of the key and the operation of the E106 relay which bridges the telephone set across the tip and ring of the trunk is sufficient to prevent a flow of ringing current in the receiver. The B75 relay releases quickly preventing a subsequent flow of ringing current in the receiver should the distant operator momentarily disconnect. If the trunk key is operated to the holding position, the telephone set is disconnected from the trunk and a retardation coil is bridged across, preventing the distant cord supervisory lamp from lighting. When the holding key is operated, the Ell relay operates disconnecting the monitoring circuit from the telephone set. Should

(4 Pages) Page #2. Issue 1 - BT-438465. February 20. 1920.

the call be incoming over a tie line, the B75 relay and #54-D retardation coil are not bridged across the trunk, but ground is applied to operate the E106 relay in series with the E179 relay by the operation of the talking key. When the flashing key is operated, the E247 relay operates, opening the ring side of the trunk and holding the E106 relay operated. The B75 relay and the #54-D retardation coil are disconnected from across the tip and ring of trunk, lighting the cord supervisory lamp. This cycle of operation reduces the click produced in the receiver when the circuit through the B75 and #54-D retardation coil is opened. When the flashing key is restored, the above cycle is reversed, releasing the E247 relay and closing the ring side of the trunk. The E247 relay is rather slow in releasing to prevent the ring side from being closed before the B75 relay and #54-D retardation coil are bridged across the tip and ring of the trunk, thereby reducing the click in the receiver. When the talking key is restored, the called supervisory lamp at the distant end lights as a disconnect signal. od Laono čilš skils Bosilskiek on byteški spod u nov šak kladskiehote, je

. hererogeneed ... of eithe ... Entered.

- 4. To make a call over a ringdown trunk or tie line, the plug of this circuit is inserted in the trunk jack, or if the tie line is key ended, the talking key is operated. The ringing key is then operated, lighting the trunk lamp at the distant end. When the talking key is operated, the telephone set is bridged across the trunk. Should the call be to an automatic office instead of the ringing key being operated, the talking key is operated and the desired number is dialed. Provide the best of a best cooks at stocking and to sait our pane
- 5. When the #137 plug of the telephone set is inserted in either pair of telephone jacks, the special E24 relay per D-14054 operates in series with the transmitter and the orimary winding of the #24 induction coil. The operation of this relay disconnects the transmitter of the special #20-CM desk stand per D-12746 and connects in that of the telephone head set. The head receiver may be used in connection with the special #20-CM desk stand by inserting the #87 cord in the telephone jacks.

efeldenen der Belsker bis 1800 bische bische beste bei e fact beste best when on the second which the set, in the set, building the set and should have be set of the भागावार अन्य वर्ग सम्बोधित के का कार्य महितादारों के उन्हें कार के प्रसाद के उन्हें के संस्थित है। Chierage and analytical making the authorizing and additional and analytic and the control of the little of the control of the

e la company de la company Esta de la company de la compan to controlly and entiremental partitions of course of the control of the con-

And the second control of the second control The state of the state of temperature and the state of th

by the of the this court of the special of the medical of the solution of the There is not profit that the real descents well also the trade a delivery as profit

cost with the construction within the was the above the first of the action, because it was the es com stands and de separatectural religion scape decisiones devision and be to with the profession to the destruction and all alleges to the second of the best of

o io signification of the contraction of the contra

There is a second of a little of the second of the second

(4 Pages) Page #3. Issue 1 - BT-438465. February 20, 1920.

.0025 ampere.

CIRCUIT REQUIREMENTS

RELEASE NON-OPERATE OP ERATE Rather slowly in local Sp1.#178 circuit at 20 volts. per Testing current agree on se studyle Testing current D-10866 .034 ampere. .047 ampere. Adjusting current Adjusting current .035 ampere. .044 ampere. In series with 350 B75 ohms and one winding of the #54-D retardation coil when shunted by the to anionis wraning other winding of the latter at 20 volts. Through relay: Through relay: Acorton antisoff Testing current Testing current .0038 amorro . . . 0025 ampere. .0052 ampere. fagrass galfauthA Adjusting current Adjusting current .019gmg 200. .0026 ampere. .0049 ampere. When applied to When applied to ring lead: ring lead: Testing current Testing current .018 ampere. .039 ampere. Adjusting current Adjusting current .019 ampere. .037 ampere. Testing current In local circuit Ell .010 ampere. at 20 volts. Adjusting current Testing current .011 ampere. .026 ampere. Adjusting current .024 ampere. Testing current In series with E179 E106 .020 ampere. relay at 20 volts. Adjusting current Testing current .021 ampere. .027 ampere. Adjusting current .026 ampere. In series with E106 E179 relay at 20 volts. Testing current Testing current .012 ampere. .022 ampere. Adjusting current . LOD - . SVD - . IV-REH Adjusting current .013 ampere. .021 ampere. Rather slowly at In local circuit at 28 volts. E247 Testing current 20 volts.

Testing current .020 amperc. Adjusting current .019 ampere. (4 Pages) Page #4. Issue 1 - BT-438465. February 20, 1920.

1797 to 7 Street	CIRCUIT REQUIR	EMENTS	
IF ALLEG		STAF 50	
OP ERATE	NON-OPERATE		
E249 Quickly in local circuit at 20 Testing curren .018 ampere. Adjusting curren .017 ampere.	t diagram actions	Rather slow: 28 volts. Testing curr .0025 amp. Adjusting columns.	rent
Spl.E24 In series with transmitter an primary windin the #24 induct coil at 20 vol Testing curren .0053 ampere. Adjusting curren .0050 ampere.	d g of ion ts. t Testing cu .0038 ampe	re. Instruc galie i current stooms 2000; e. Instruc galie i bA 2019ghe 2000.	
The lead: The sting current Log supere. Log supere. Log supere.		of believe some to the interest the control of the	
	Incres gaisect .orogae Oio. Incress gaiseuthk .orogae Iio.	incrio lecel di se allo volta. Testing current se singere. Adjusting current Adjusting current	fie
	Testing carrent .020 superc. Adjusting carrent .021 superc.	relay at 20 valts. relay at 20 valts. Resting corrent Adjusting corrent .025 amosrc.	1106
HBH-VI CVP GBJ. 2/20/22.	The sting carront 1012 ampero. Adjusting carront .015 ampero.	In acries with 1106 relay at 20 relay at 20 relats. Testing carrent Adjusting carrent .022 andere.	6413

SUMPRIME BESTERNAND

to give to tantes Pesting carrons .0026 arpers.

te discrib (ecol mi .BJIov OS .orogeme Ono.